

Outline


- **Efficient Characterization of the Dynamics of Systems**
- **L-C Resonator**
- **R-C Low-Pass / C-R High Pass Filters**
- **Example: Fast Timing Signal from a Slow Rising Signal**
- **Digitized Front-End**
- **Summary**

→ ...hiskp.uni-bonn.de → lectures → archive



- Electronics for Physicists (in SS)
- Advanced Electronics and Signal Processing (in WS)

Electronics II

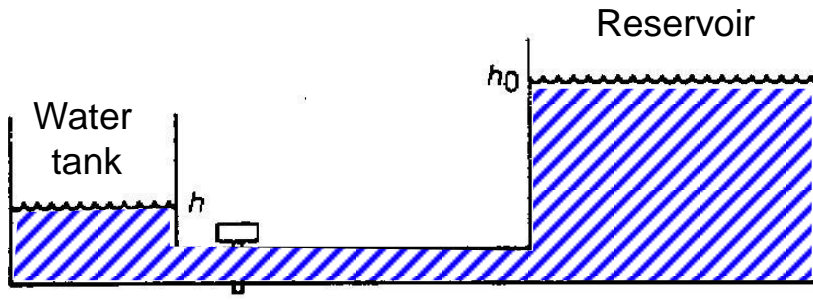
– Efficient Characterization of the Dynamics of Systems –



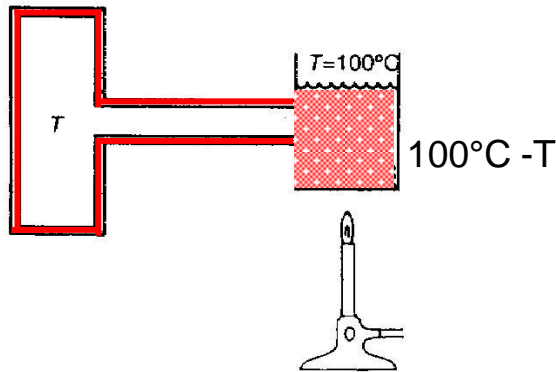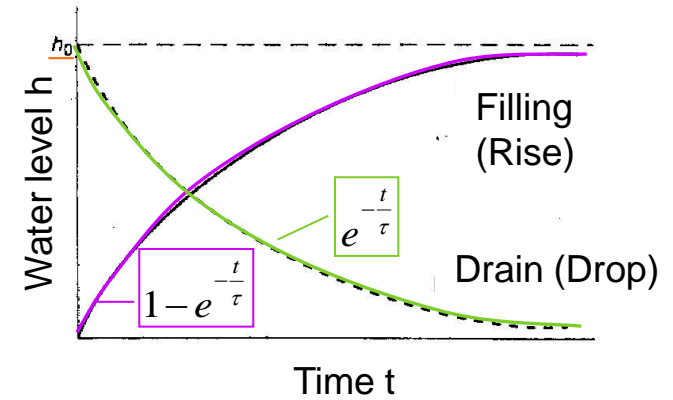- The water tank is filled from a reservoir of unlimited capacity;
- The water level approaches **exponentially** h_0 .








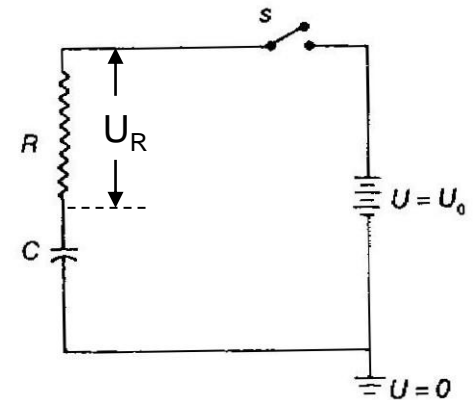
The temperature of a piece of metal approaches exponentially 100°C .



The voltage across the capacitor C approaches exponentially U_0

Electronics II

– Efficient Characterization of the Dynamics of Systems –

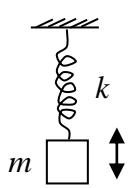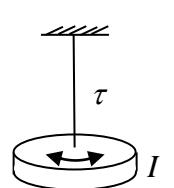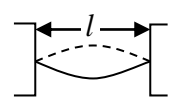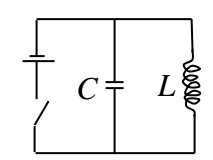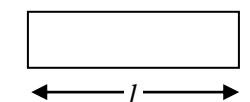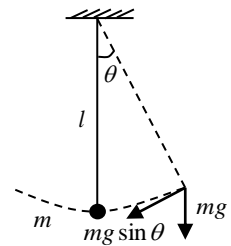
	Oscillator	Torsion Pendulum	String	Oscillatory Circuit	Echo Chamber	Pendulum
Excitation	 <p>Pull down mass and release it</p>	 <p>Turn disk and let loose</p>	 <p>Pluck string</p>	 <p>Close switch, after that open. Charge oscillates through the coil and between the disks of the capacitor</p>	 <p>Make a banger explode in a chamber</p>	 <p>Move mass and let loose</p>
Eigen frequency	$\frac{1}{2\pi} \sqrt{\frac{k}{m}}$	$\frac{1}{2\pi} \sqrt{\frac{\tau}{I}}$	$\frac{1}{2l} \sqrt{\frac{Z}{\mu}}$	$\frac{1}{2\pi} \sqrt{\frac{1/C}{L}}$	$\frac{1}{4l} \sqrt{\frac{E}{\rho}}$	$\frac{1}{2\pi} \sqrt{\frac{mg/l}{m}} = \frac{1}{2\pi} \sqrt{\frac{g}{l}}$
Rigidity	Spring constant k	Torsion constant τ of the wire	Pulling force Z in the string	Reciprocal of the capacity 1/C	Adiabatic volume elasticity E of the gas inside the chamber	Restoring force per displacement, mg/l
Inertia	Mass	Moment of inertia I of the disk	Lengths density μ of the string	Inductivity of the coil	Density ρ of the gas in the chamber	Mass

Electronics II

– Efficient Characterization of the Dynamics of Systems –



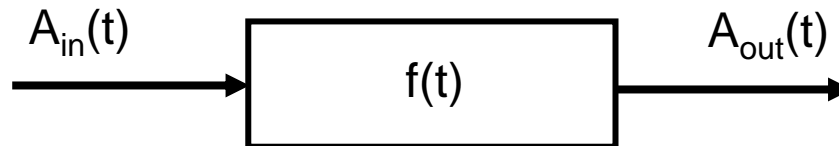Refinery
Aeroplane
Musical instrument
Electronic Circuit
Nucleus




$$\int_0^t A_{in}(t - \tau) \cdot f(\tau) d\tau = A_{out}(t)$$

Electronics II

– Efficient Characterization of the Dynamics of Systems –

The Laplace Transform

- Is a „generalized“ Fourier Transform $f(t) \rightarrow F(s)$; $s = i\omega + \varrho$
- „Algebraizes“ linear differential equations (that represent the dynamics of systems with concentrated energy „reservoirs“ like L, C, ...)
- A convolution in the time domain corresponds to a multiplication of the Laplace transform

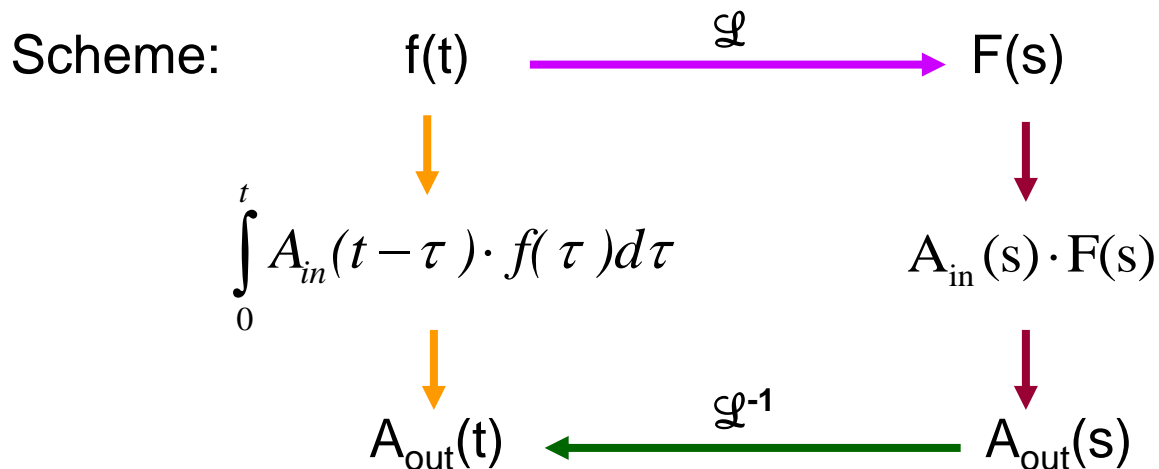




Electronics II

– Efficient Characterization of the Dynamics of Systems –

$\mathbf{F(s)} = \int_0^{\infty} e^{-st} F(t) dt$	$\mathbf{f(t)}$	Remark
$a F_1(s) + b F_2(s)$	$a f_1(t) + b f_2(t)$	Linearity
$s F(s) - f(0)$	$f'(t)$	Derivative
$s^n F(s) - s^{(n-1)} f(0) - s^{(n-2)} f'(0) \dots - f^{(n-1)}(0)$	$f^{(n)}(t)$	n^{th} derivative
$\frac{1}{s-a}$	e^{at}	
$\frac{F(s)}{s}$	$\int_0^t f(\tau) d\tau$	Integral
$\frac{F(s)}{s^n}$	$\int_0^t \dots \int_0^t f(\tau) d\tau^n = \int_0^t \frac{(t-\tau)^{n-1}}{(n-1)!} f(\tau) d\tau$	n-fold integral
$A(s) \cdot F(s)$	$\int_0^t A(t) \cdot f(t-\tau) d\tau$	Convolution in the time domain

Electronics II

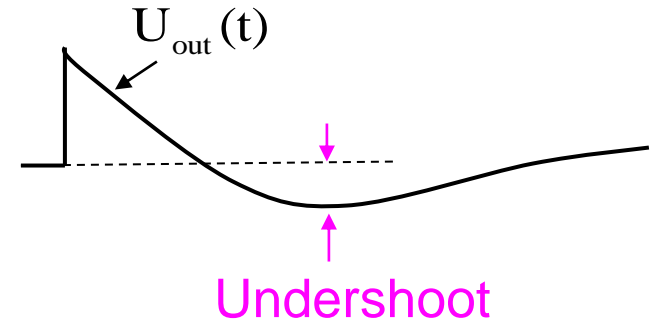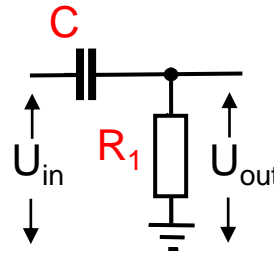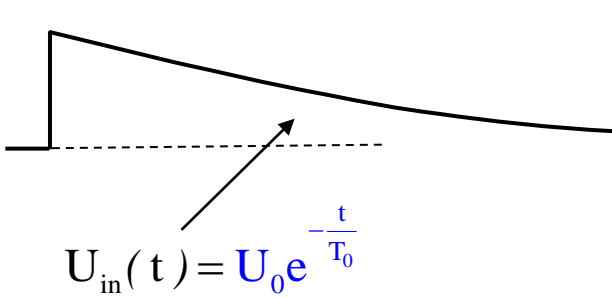– Efficient Characterization of the Dynamics of Systems –



$$U_{in}(s) = U_0 \frac{1}{s + 1/T_0}$$

$$T(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{R_1}{\frac{1}{sC} + R_1}$$

$$U_{in}(s) \cdot T(s) = U_0 \frac{s}{(s + 1/T_0)(s + 1/CR_1)} = U_{out}(s)$$


$$U_{out}(t) = U_0 \frac{1}{(CR_1 - T_0)} \left(CR_1 e^{-\frac{t}{T_0}} - T_0 e^{-\frac{t}{CR_1}} \right)$$

Electronics II


– Efficient Characterization of the Dynamics of Systems –

- For physically feasible systems applies: $n \leq m$

$$T(s) = \frac{U_{\text{out}}(s)}{U_{\text{in}}(s)} = \frac{\sum_{\ell=0}^n b_{\ell} \cdot s^{\ell}}{\sum_{k=0}^m a_k \cdot s^k} = k \frac{\prod_{\ell=1}^n |s - s_{N_{\ell}}|}{\prod_{k=1}^m |s - s_{P_k}|} \cdot e^{i\left(\sum_{\ell=1}^n \psi_{\ell} - \sum_{k=1}^m \varphi_k\right)}$$

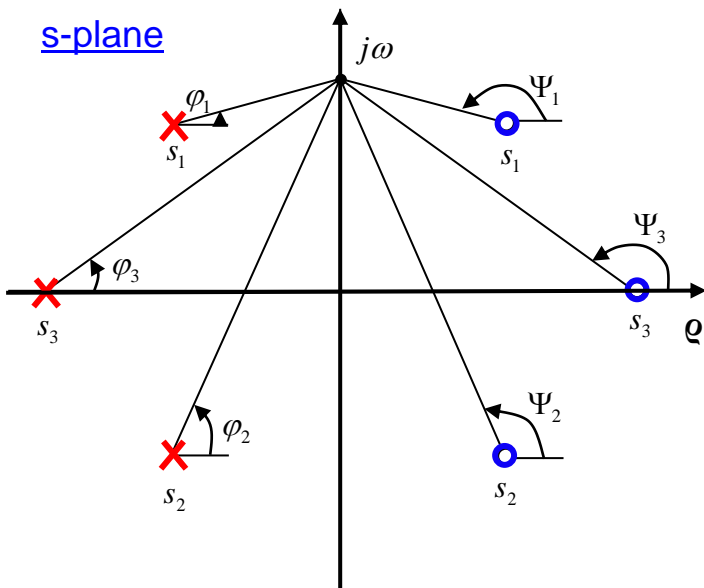


Pole/Zero Applet

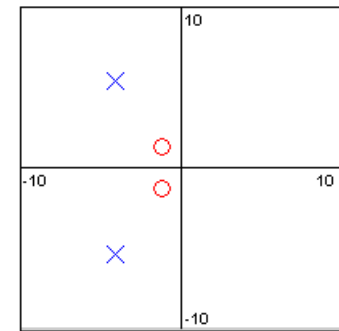

Electronics II

– L-C Resonator –

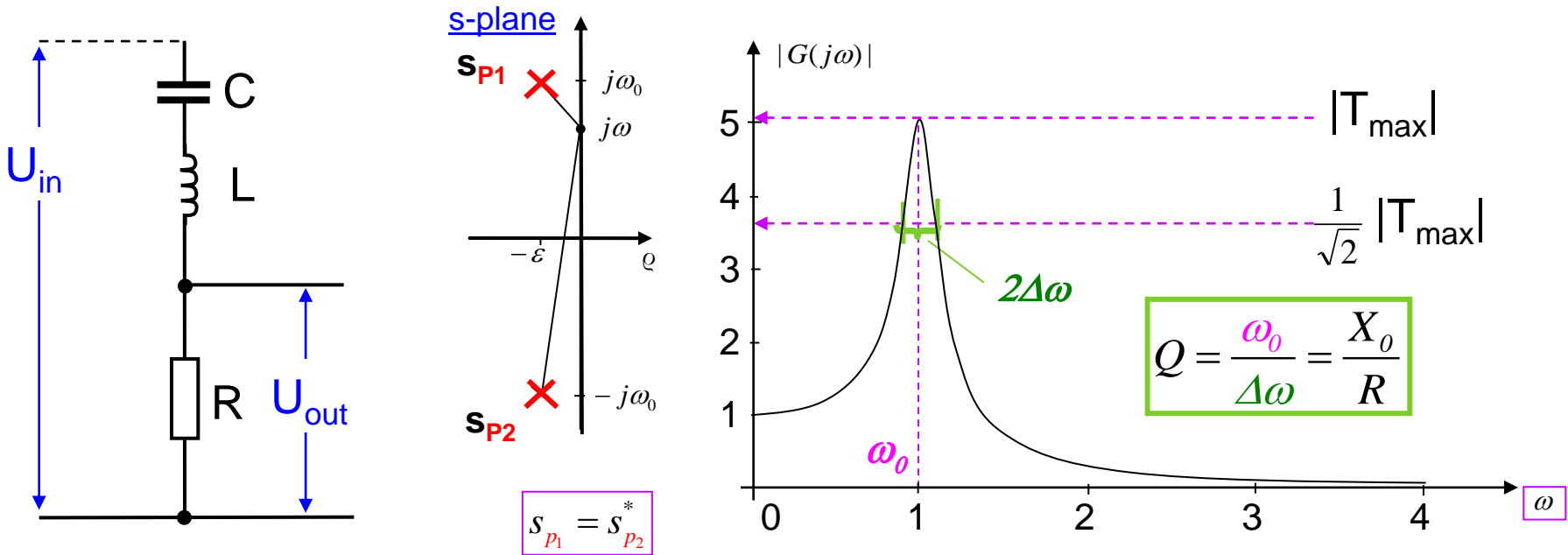
P/N-Scheme of a system with frequency sensitive behaviour:



$$T(s) = \frac{1}{1 + Q \cdot \left(\frac{s}{\omega_0} + \frac{\omega_0}{s} \right)} \xrightarrow[\omega = \omega_0 + \delta\omega, \rho = 0]{\text{Small bandwidth approximation}} \frac{1}{1 + i \frac{\omega - \omega_0}{\Delta\omega}} = \frac{\Delta\omega}{\Delta\omega + i(\omega - \omega_0)}$$

Electronics II

– L-C Resonator –

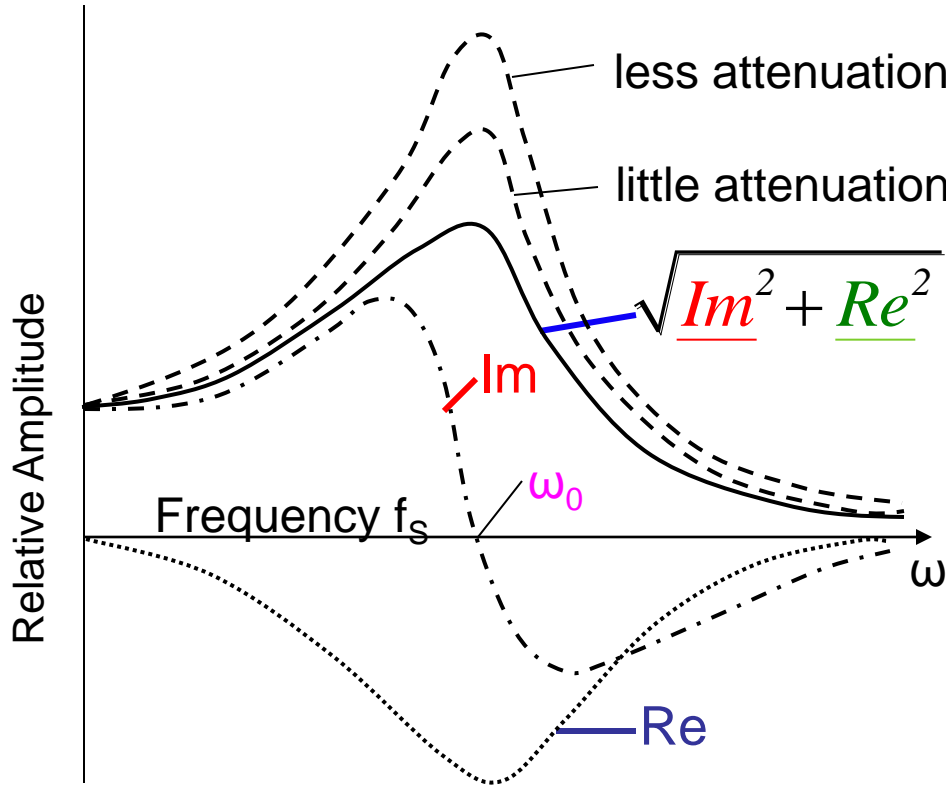

$$\omega_0 = \sqrt{\frac{1}{LC}} \quad X_0 = \sqrt{\frac{L}{C}}$$


$$Q = \frac{X_0}{R}$$

Examples

Examples	Q
L-C oscillator circuit	100
Soil for earthquake waves	250-1400
Tuning fork	$4,5 \cdot 10^4$
Plucked violin string	10^3
Cavity resonator	10^4
Quartz crystal	10^6
Excited atom	10^7

Electronics II

– L-C Resonator –

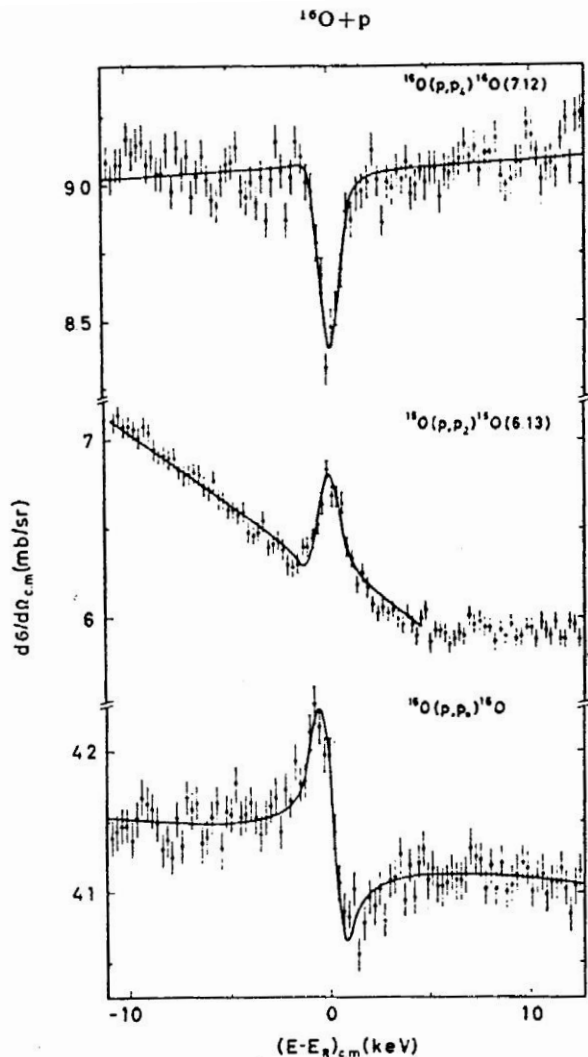

- Excitation function of $^{16}\text{O}(p,p)^{16}\text{O}$; Resonance in ^{17}F .
- The solid curve is the theoretical fit.
- Expanding the small band approximation of the standard form of a resonance by \hbar leads to the Breit-Wigner resonance equation:

$$S_{\text{LJ}}^{\text{R}} = S_{\text{LJ}} - i \frac{\Gamma_{\text{p}}}{E - (E_0 - i\Gamma/2)} \exp\{2i(\mu_{\text{LJ}} + \sigma_{\text{L}} + \Phi^{\text{R}})\}$$

$$\propto \frac{\text{const.}}{\Gamma/2 + i(E - E_0)} \cdot e^{i\varphi}$$

$$\theta_{\text{lab}} = 168,3^\circ$$

$$E_0 = 11193 \pm 2,3 \text{ keV}$$


$$\Gamma = 0,20 \pm 0,04 \text{ keV}$$

From: Nucl. Phys. A263 (1976) 460


Electronics II

– L-C Resonator –

Dipol-Rotation

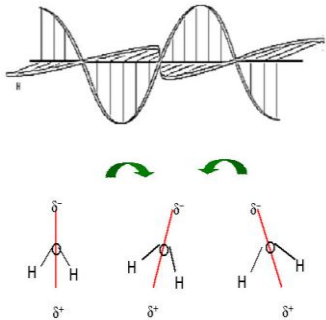

Dielectric Absorption of Water and Ice (Microwave Oven)


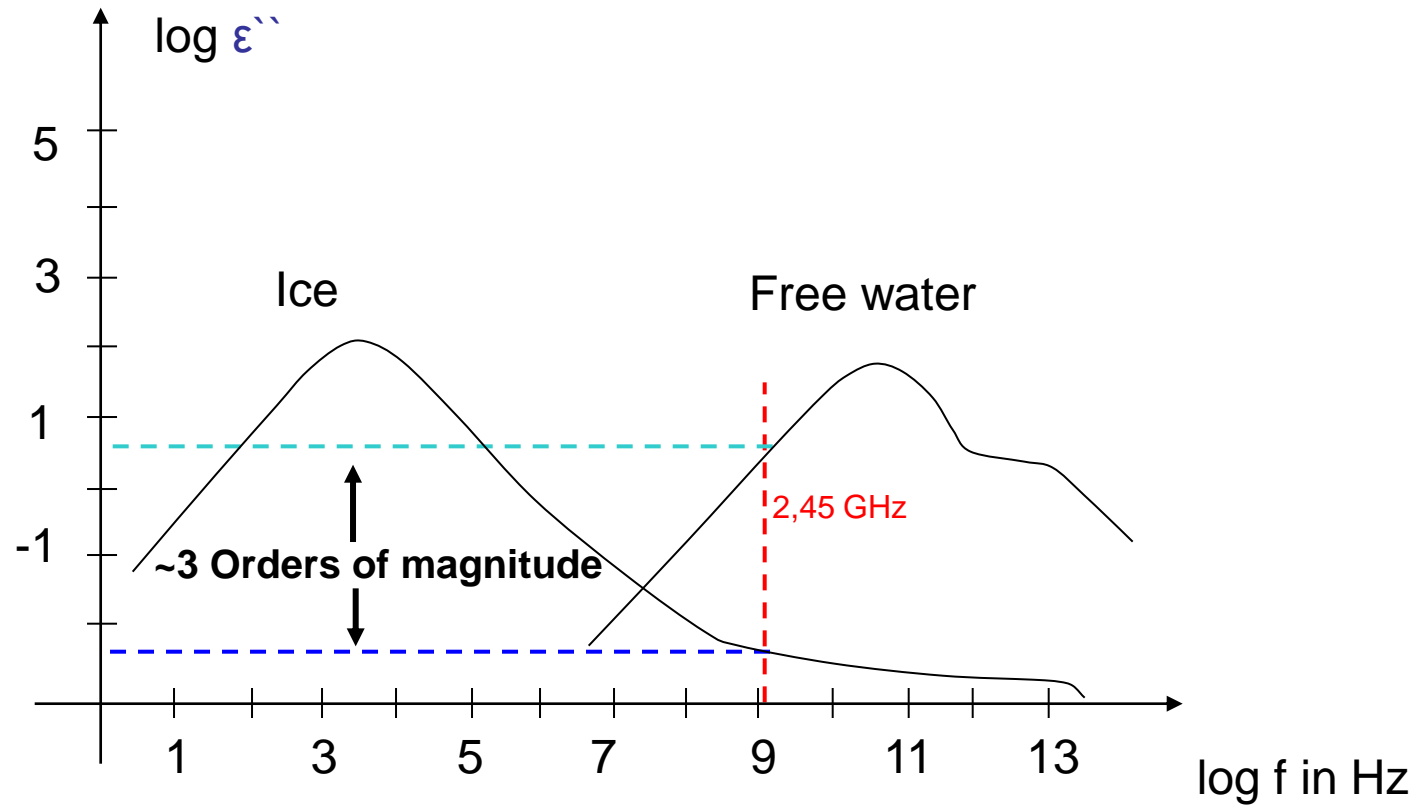


Electronics II

– L-C Resonator –

Nuclear Magnetic Resonance → Magnetic Resonance Tomography

90° „Puls“ for magnetization \vec{M}

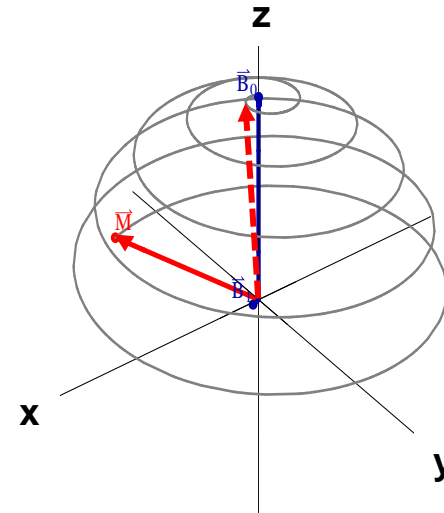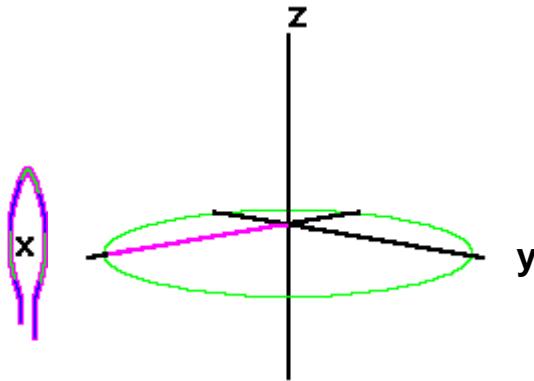


Lamor frequency for protons: $42.577\,478\,92(29)$ MHz / Tesla = $\gamma_p/2\pi$

γ_p , the gyromagnetic ratio of a proton, is a **fundamental constant**.

Electronics II


– R-C Low-Pass / C-R High Pass Filters –

C-R Highpass

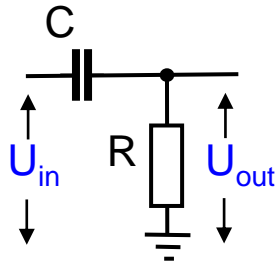


$$T(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{R}{R + \frac{1}{sC}} = \frac{sCR}{sCR + 1}$$


s-plane

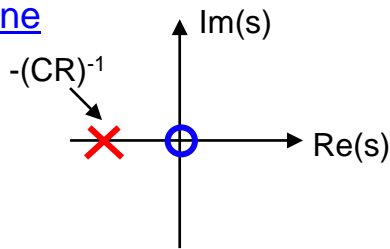


R-C Lowpass

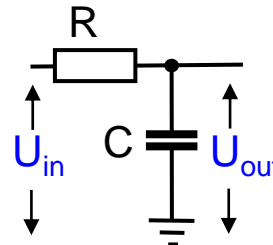
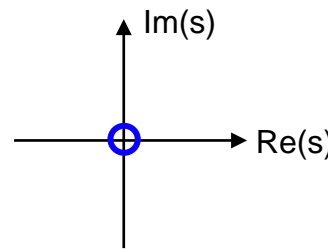
$$T(s) = \frac{U_{out}(s)}{U_{in}(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{sCR + 1} \dots = \frac{1}{(sCR + 1)^2} \dots = \frac{1}{(sCR + 1)^3}$$



...

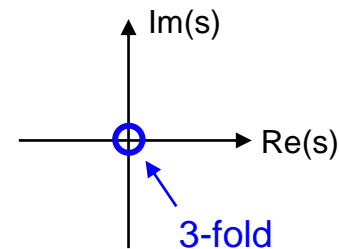


C-R – (R-C)ⁿ Combination:

$$T(s) = \frac{sCR}{(1 + sCR)^{n+1}}$$

Electronics II


– Fast Timing Signal from a Slow Rising Signal –

CsJ Signal

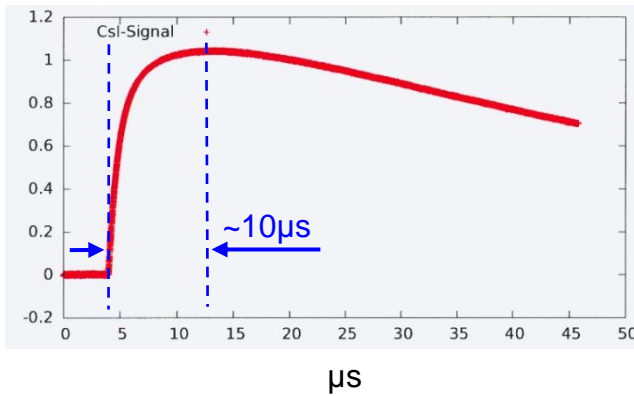

Approximated Signal
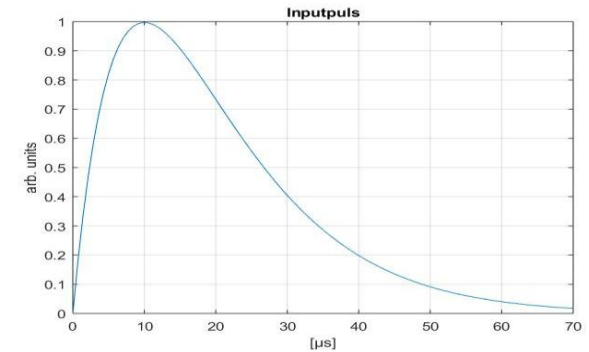
$$U_{in}(t) = A \cdot t \cdot e^{-t/Tau}$$
$$U_{in}(s) = \frac{A}{(s + 1/Tau)^2}$$




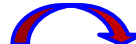
Task:


Generate a **fast timing signal within 300ns** by a C-R – (R-C)ⁿ Filter

Electronics II

– Fast Timing Signal from a Slow Rising Signal –

Define Figure of Merit (FM)

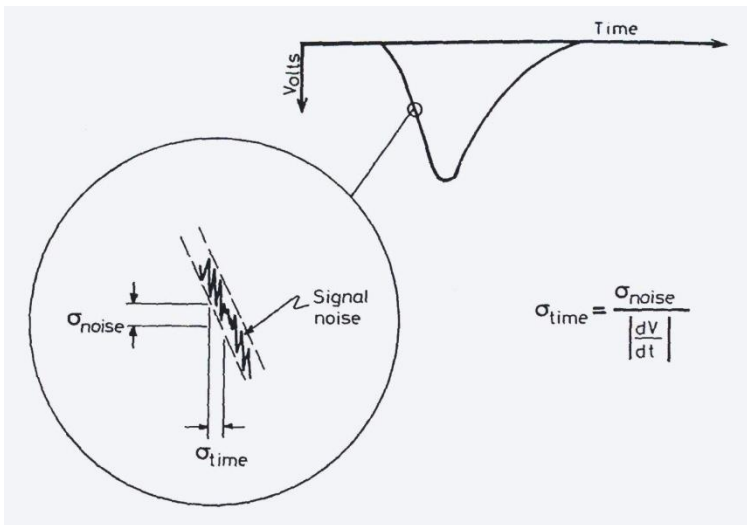- The noise should be reduced substantially :  Reduce bandwidth (BW)
- The slope should be as steep as possible to become insensitive to noise :  Trigger at maximum steepness within 300ns



$$\Rightarrow \text{FM} = \frac{dU_{\text{out}} / dt}{\text{BW}}$$

Electronics II

– Fast Timing Signal from a Slow Rising Signal –







Code Examples

```
29
30 % Generate plots for the filters
31 for i = 2:4
32     clear s t U_in U_out dU_out ddU_out LTI f y_in y_out x LT
33     syms s t U_in U_out dU_out ddU_out LTI f y_in y_out x LT
34     str = strcat('Data for: ', txt(i-1))
35     fprintf('\n') % line feed / carriage return
36     U_in = A*t*exp(-t/Tau);
37     LTI = s*CR/(1+s*CR)^i; % Linear time invariant filter
38     LTI6=10^-6*s*CR/(1+s*CR/10^6)^i; % save LTI for Bode Plots
39
40 % Calculations of output signal and its derivative
41 f = LTI*laplace(U_in);
42 U_out = ilaplace(f);
43 dU_out = diff(ilaplace(f), t);
44
45 % Calculate in- and outputsignal for plots
46 x = logspace(-2, 2, 100);
47 xout = x;
48 y_in = U_in;
49 y_in = subs(y_in, t, x); % substitute t by x for y_in
```

```
110
111 % BodePlot of the bandwidth
112
113 [nums, dens] = numden(LTI6); % determine vector representation of LTI6
114 num = sym2poly(nums);
115 den = sym2poly(dens);
116 LT = tf(num, den); % determine zthe transferfunction of the filters
117 figure;
118 opts = bodeoptions('cstprefs');
119 opts.FreqUnits = 'MHz';
120 opts.Grid = 'on';
121 opts.XlimMode = 'auto';
122 opts.YlimMode = 'manual';
123 opts.YLim = {[ -80, 20]; [ -270, 90]};
124 opts.PhaseUnits = 'deg';
125 opts.Title.FontSize = 12;
126 Txt = strcat('Bode Plot of ', txt(i-1));
127 opts.Title.String = Txt;
128 h = bodeplot(LT, opts);
```

Electronics II

– Fast Timing Signal from a Slow Rising Signal –

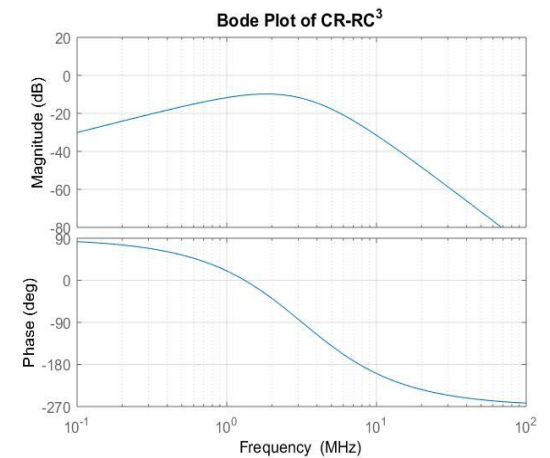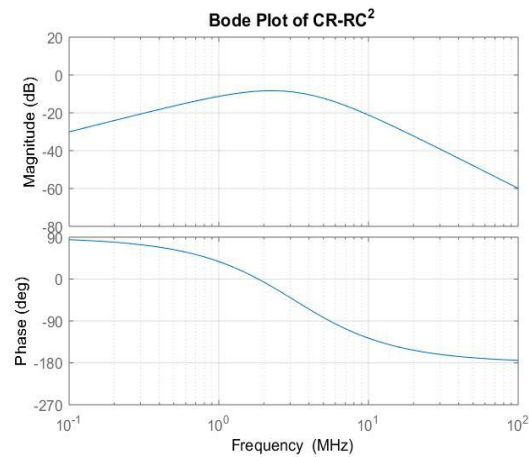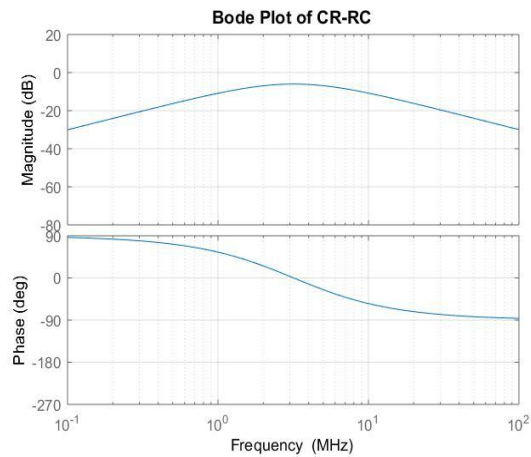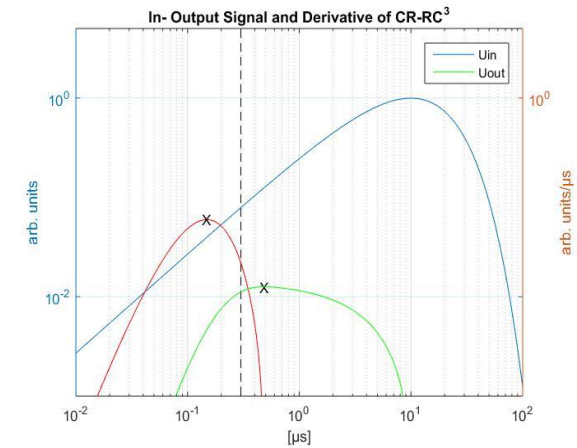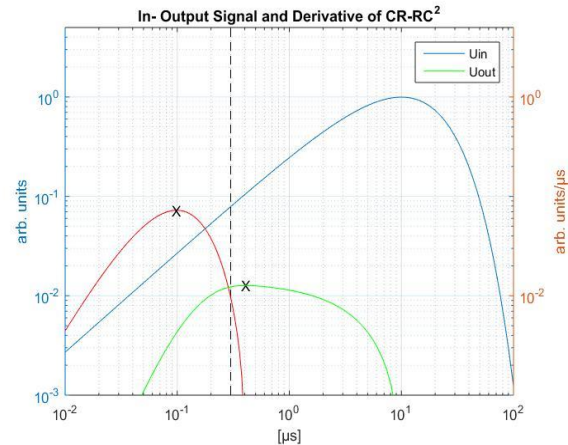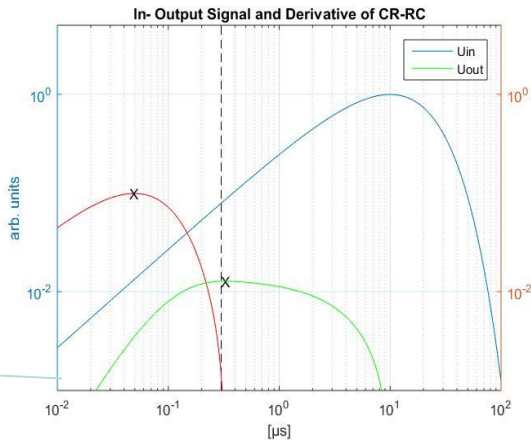

Electronics II

– Fast Timing Signal from a Slow Rising Signal –

Results

CR = 50ns	Uout		dUout/dt		Fmin	Fmax	Bandwidth	FM
	Ampl.	tmax [ns]	Ampl.	tmax [ns]				
CR – CR	0.013	0.327	0.099	0.050	1.320	7.693	6.373	0,016
CR -CR ²	0.013	0.412	0.072	0.099	0.998	4.504	3.506	0,021
CR - CR ³	0.013	0.488	0.060	0.149	0.836	3.445	2.609	0,023

The trigger time should be set @ ~150ns for a C-R – (C-R)³ filter to be **most insensitive to noise**.

Electronics II

– Digitized Front-End –

Tasks of Digitized Front-End:

- Shapes signals (reduce noise)
- Amplifies signal
- First level trigger (Discriminator)
- Provides timing signal
- Provides time stamp
- Suppresses Zeros


Necessary for Digitized Front-End:

- **F**ast **A**nalogue → **D**igital **C**onverter
- **R**eal **T**ime (**K**ernel) operating system
- Special (**H**arvard) processor **a**rchitecture, that allows summing & multiplication within 1 clock cycle with:
 - **D**igital **S**ignal **P**rocessor Slices
 - Gigabit Tranceivers
 - Dual ported memory
 - Ring buffers
- Calculations utilize special Laplace Transform:
z-Transform:
For a stable system → Poles inside unit circle


Electronics II

– Digitized Front-End –


Low- Highpass

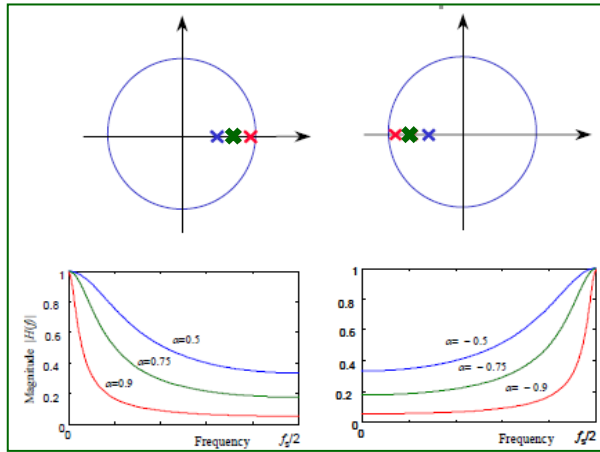


High- Lowpass

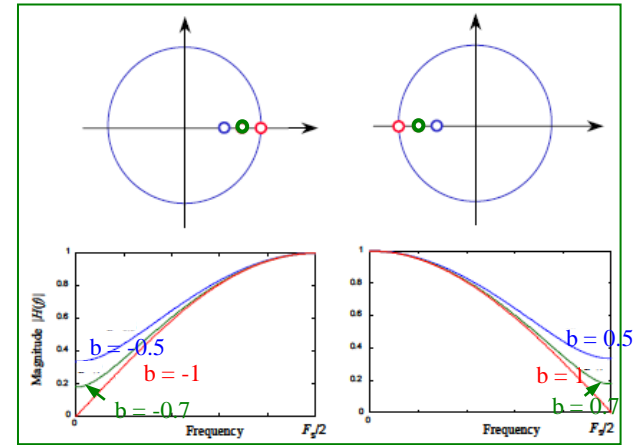


Resonators

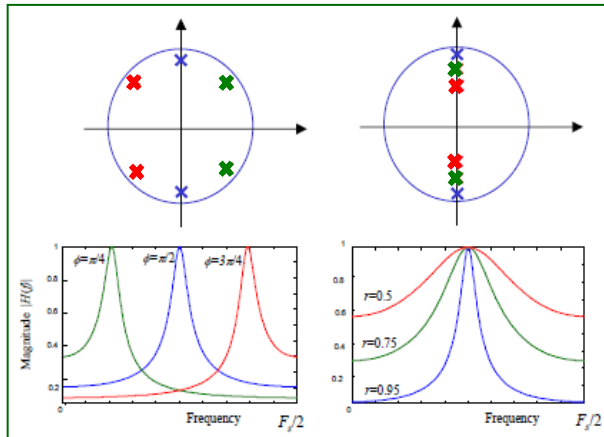

Notch Filter

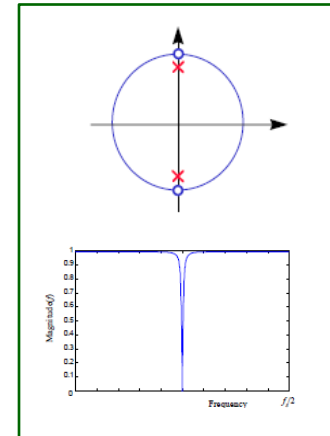

3-Tap Moving Average

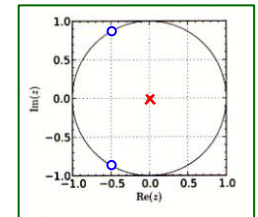

Electronics II

– Digitized Front-End –

Hardware Realization

ASIC

Application Specific
Integrated Circuit

FPGA

Field Programmable
Gate Array

ASIC vs. FPGA

	ASIC	FPGA
Cost per chip	low	various
NRE cost (one time production cost)	(very) high	none
Power efficiency	+++	-
Area efficiency	+++	--
Performance vs. power, area	+++	--
Flexibility	---	+++
Development/programming complexity	very high	various

ASICs used when

- Highest performance
- High volume production
- Power & area constraints
- Special requirements
 - Analog + digital functions
 - Radiation tolerance
 - ...

FPGAs used when



- Max. flexibility
- Low – medium volume production
- Power & area not critical
- Digital only

Introduction to FPGAs, H. Krüger, Bonn University, 2015

Electronics II

– Digitized Front-End –

- Test system for ATLAS FE-I4 pixel chip

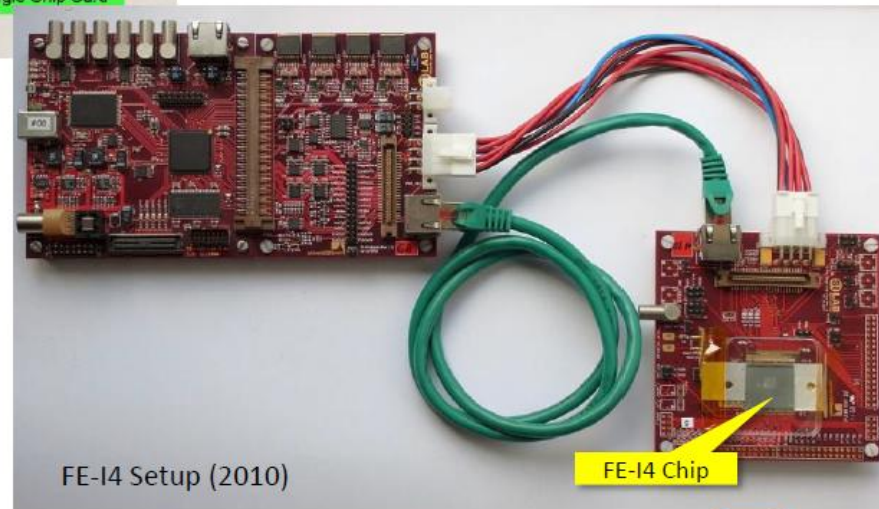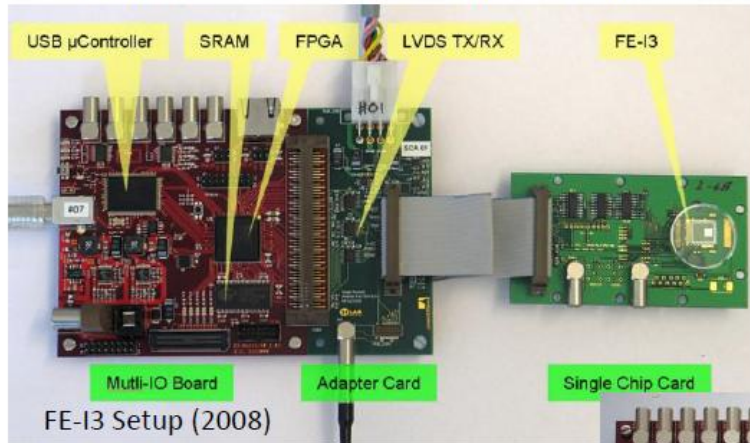


Introduction to FPGAs, H. Krüger, Bonn University, 2015



Electronics II

– Digitized Front-End –

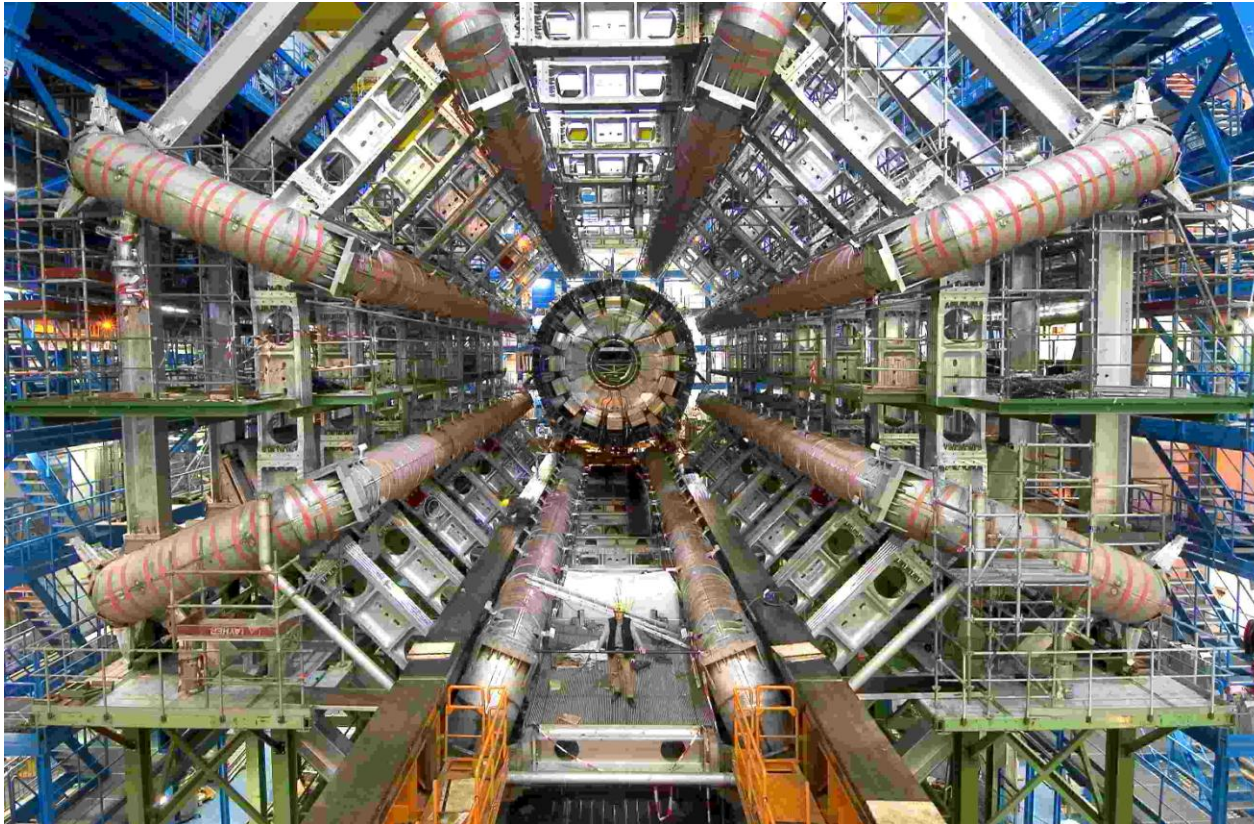- ATLAS Pixel detector read-out
 - Pixel Module → back of crate card (BOC) → read out driver (ROD)



Introduction to FPGAs, H. Krüger, Bonn University, 2015



Electronics II

– Summary –

- The **dynamics of systems** with concentrated energy reservoirs is represented by **Linear Differential Equations (LDE)**.
- The **Laplace Transform** is a standard means to **solve LDEs & convolutions**.
- **Poles & Zeros** in the complex s-plane **represent** concisely **the dynamics** of a system.
- **MRI** is based on the **precise knowledge of** the gyromagnetic ratio γ of particles.
- The **z-Transform** accomplishes in the **digitized world** what the **Laplace Transform** does in the **analogue world**.
- **Digitized signal processing** is governed by the hardware performance of **fast ADCs, ASICs, FPGAs & DSPs**.